

Control Systems

G V V Sharma*

CONTENTS

1	Feedback Voltage Amplifier: Series-Shunt	1
2	Feedback Current Amplifier: Shunt-Series	1
2.1	Ideal Case	1
2.2	Practical Case	1
3	Feedback Current Amplifier: Example	1
4	Feedback Transconductance Amplifier: Series-Series	1
5	Op-Amp RC Oscillator Circuit	1

Abstract—This manual is an introduction to control systems in feedback circuits. Links to sample Python codes are available in the text.

Download python codes using

```
svn co https://github.com/gadepall/school/trunk/
control/feedback/codes
```

1	FEEDBACK VOLTAGE AMPLIFIER: SERIES-SHUNT
2	FEEDBACK CURRENT AMPLIFIER: SHUNT-SERIES
2.1	Ideal Case
2.2	Practical Case
3	FEEDBACK CURRENT AMPLIFIER: EXAMPLE
4	FEEDBACK TRANSCONDUCTANCE AMPLIFIER: SERIES-SERIES
5	OP-AMP RC OSCILLATOR CIRCUIT

5.1. For the circuit in Fig. 5.1.1 (ignore the amplitude stabilization circuitry), find the loop gain GH by breaking the circuit at node X.

5.2. **Solution:** The equivalent control system representation of Oscillator circuit is shown in

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

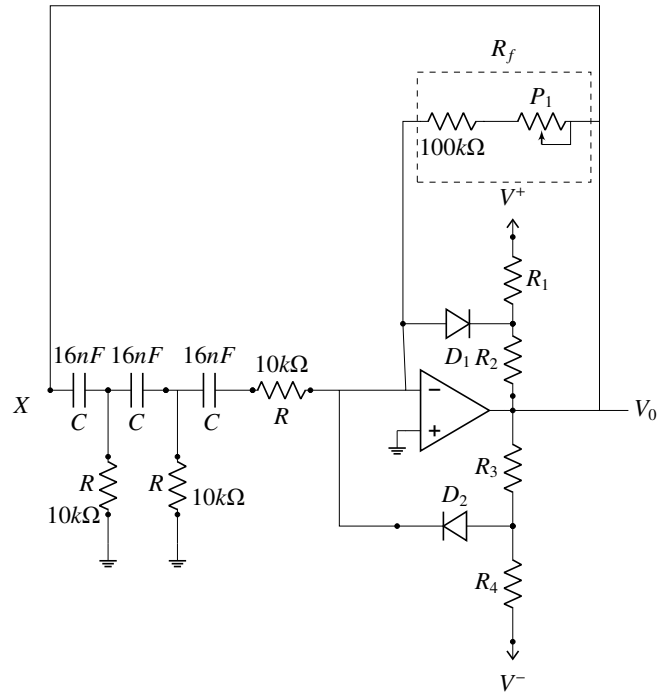


Fig. 5.1.1

Fig. 5.2.2. Oscillator circuits do not have input. After removing the amplitude stabilization

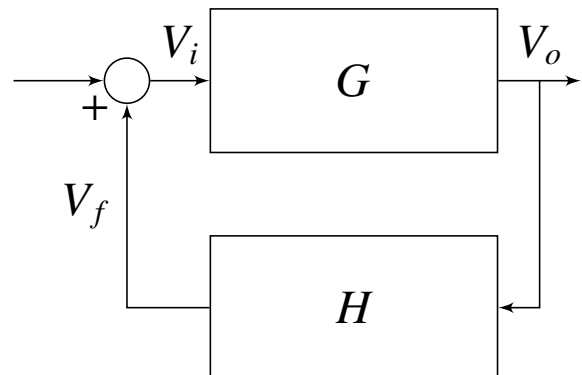


Fig. 5.2.2

circuitry, when we break the loop at X, from Fig. 5.2.3 the value of gain

$$GH = \frac{v_o(j\omega)}{v_x(j\omega)} \quad (5.2.1)$$

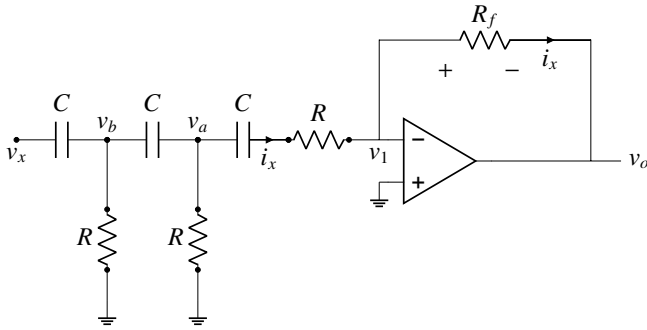


Fig. 5.2.3

$$v_1 = 0 \quad (5.2.2)$$

$$\Rightarrow v_o = -i_x R_f \quad (5.2.3)$$

$$v_a = \left(\frac{1 + sRC}{sC} \right) i_x \quad (5.2.4)$$

$$\Rightarrow v_b = \left(R + \frac{3}{sC} + \frac{1}{s^2 C^2 R} \right) i_x \quad (5.2.5)$$

$$\Rightarrow v_x = \left(R + \frac{6}{sC} + \frac{5}{s^2 C^2 R} + \frac{1}{s^3 C^3 R^2} \right) i_x \quad (5.2.6)$$

$$\Rightarrow \frac{v_x}{i_x} = \left(R + \frac{6}{sC} + \frac{5}{s^2 C^2 R} + \frac{1}{s^3 C^3 R^2} \right) \quad (5.2.7)$$

From (5.2.3)

$$\frac{v_x}{v_o} = -\frac{R}{R_f} \left(1 + \frac{6}{sCR} + \frac{5}{s^2 C^2 R^2} + \frac{1}{s^3 C^3 R^3} \right) \quad (5.2.8)$$

$$\Rightarrow \frac{v_o}{v_x} = -\frac{R_f s^3 C^3 R^3}{R(s^3 C^3 R^3 + 6s^2 C^2 R^2 + 5sCR + 1)} \quad (5.2.9)$$

Substituting $s = j\omega$ gives us the transfer function

$$\frac{v_o}{v_x} = GH = \frac{\omega^2 C^2 R_f R}{(5 - \omega^2 C^2 R^2) + j(6\omega CR - \frac{1}{\omega CR})} \quad (5.2.10)$$

5.3. Find frequency of oscillation f_0 .

5.4. **Solution:** For system to oscillate at a frequency

ω_0 ,

$$L(j\omega_0) = G(j\omega_0)H(j\omega_0) = 1 \quad (5.4.1)$$

$$\Rightarrow \angle(G(j\omega_0)H(j\omega_0)) = 0 \quad (5.4.2)$$

$$\Rightarrow 6\omega_0 CR = \frac{1}{\omega_0 CR} \quad (5.4.3)$$

$$\Rightarrow \omega_0 = \frac{1}{\sqrt{6}CR} \quad (5.4.4)$$

$$\Rightarrow \omega_0 = 2551.55 \text{ rad/sec} \quad (5.4.5)$$

$$\Rightarrow f_0 = 406.1 \text{ Hz} \quad (5.4.6)$$

5.5. Find R_f for oscillation to begin.

5.6. **Solution:** From (5.4.1)

$$\text{Re}(G(j\omega_0)H(j\omega_0)) = 1 \quad (5.6.1)$$

$$\Rightarrow \frac{R_f \omega_0^2 C^2 R}{5 - \omega_0^2 C^2 R^2} = 1 \quad (5.6.2)$$

$$\Rightarrow R_f = 29R \quad (5.6.3)$$

$$\Rightarrow R_f = 290 \text{ k}\Omega \quad (5.6.4)$$

Thus, for the oscillations to begin,

$$R_f \geq 290 \text{ k}\Omega \quad (5.6.5)$$

5.7. Tabulate your results.

5.8. **Solution:** See table 5.8

Parameter	Value
ω_0	2551.55 rad/s
f_0	406.1 Hz
R_f	290k Ω

TABLE 5.8: calculated parameters

5.9. Verify results using Spice Simulation.

5.10. **Solution:** Following readme provides instructions for simulation in spice

codes/ee18btech11050/spice/README.md

The following netlist simulates the given circuit in 5.1.1

codes/ee18btech11050/spice/
ee18btech11050_sim.net

The following code plots the oscillator output from spice simulation, which is shown in fig 5.10.4

```
codes/ee18btech11050/spice/
ee18btech11050_sim.py
```

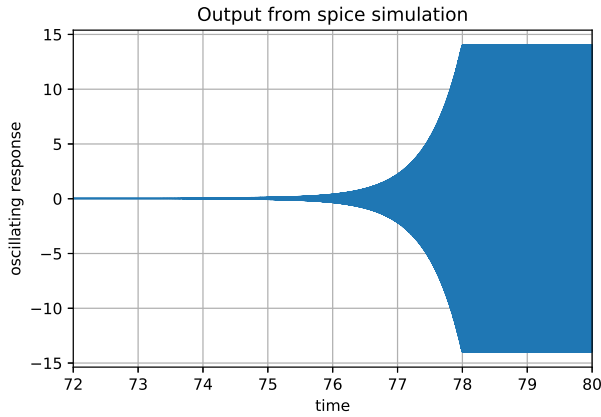


Fig. 5.10.4

The following code plots a part of spice output generated above, where a sinusoidal output can be clearly observed shown in fig 5.10.5

```
codes/ee18btech11050/spice/
ee18btech11050_sim2.py
```

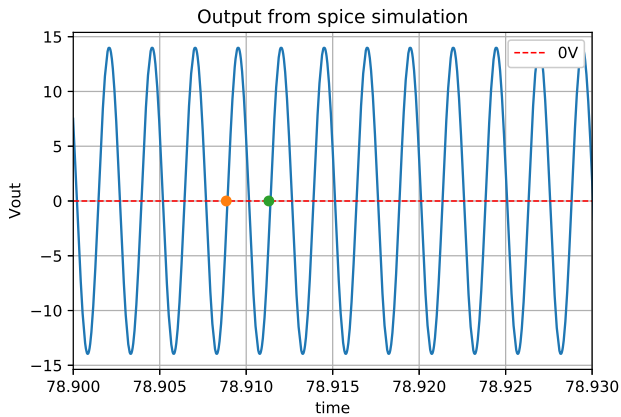


Fig. 5.10.5

From fig 5.10.5, time period is calculated from one cycle:

$$T = 78.91131 - 78.908846 = 0.002464 \text{ sec} \quad (5.10.1)$$

$$\Rightarrow f = 405.844 \text{ Hz} \quad (5.10.2)$$

Hence frequency is verified through spice simulation.